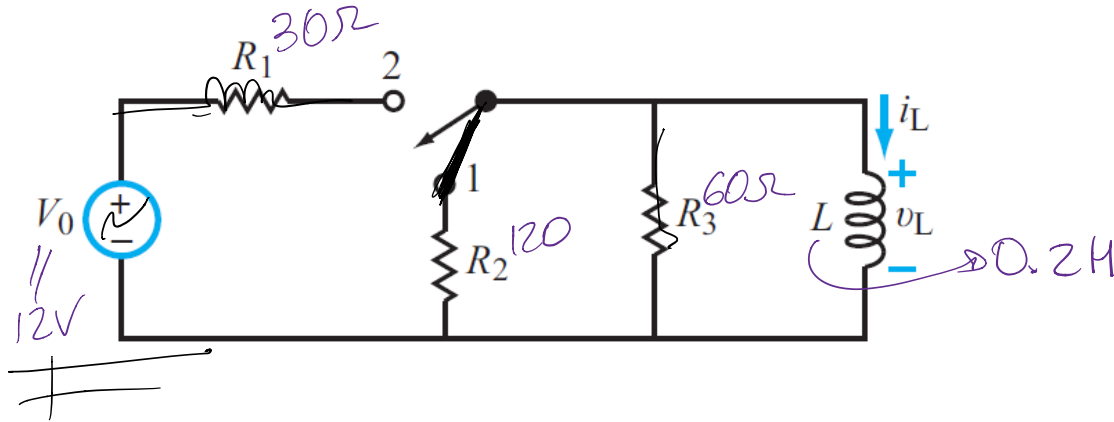


MT2 → Nov, 15 5:30 - 6:50 pm.
Modules 6-9.

MT2 Review

The switch was in position 1 for a long time, then at $t = 0$ was moved to position 2.

Given that $V_0 = 12\text{ V}$, $R_1 = 30\ \Omega$, $R_2 = 120\ \Omega$, $R_3 = 60\ \Omega$, and $L = 0.2\text{ H}$, determine $v_L(t)$ and $i_L(t)$





Assignment Project Exam Help

$$i_L(t) = i_L(\infty) + (i_L(0^-) - i_L(\infty))e^{-t/\tau}$$

<https://powcoder.com>

$$\tau = L / R_{EQ}$$

Add WeChat powcoder

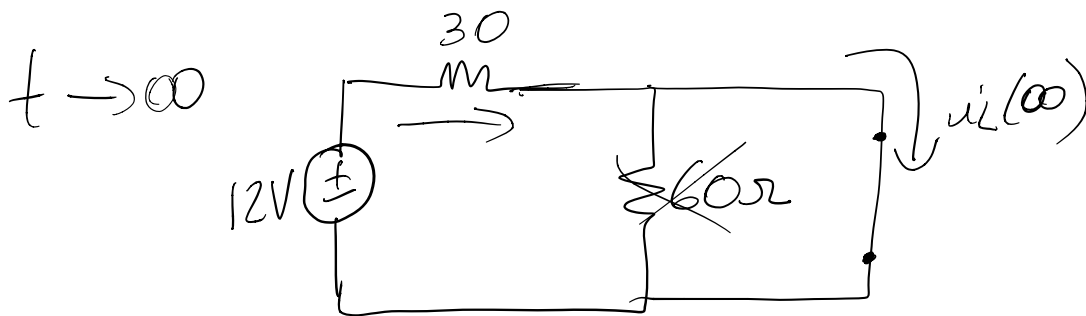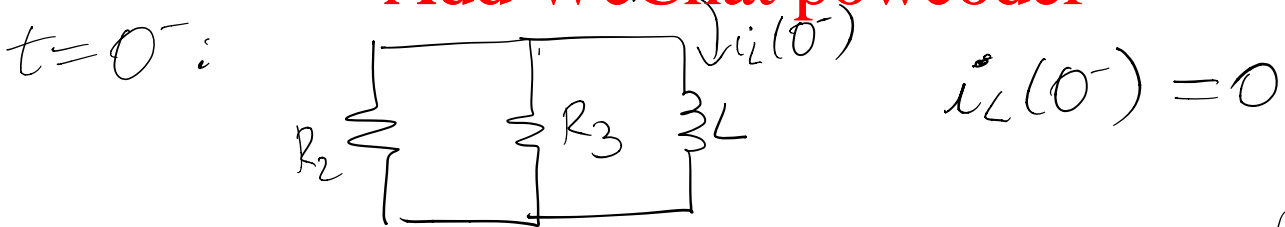


$$v_L(t) = L \frac{di_L(t)}{dt} \quad @ \text{ DC steady-state } \quad \frac{di_L}{dt} = 0$$

$$v_L(t) = 0 = \text{short-circuit}$$

$$i_L(\infty) = \frac{12}{30} = 0.4 \text{ A}$$

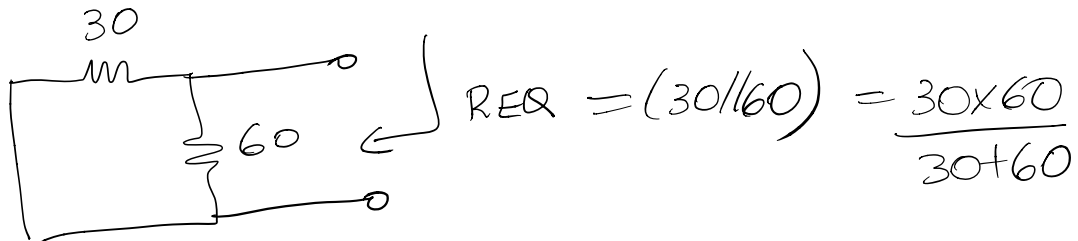To find τ , we need R_{EQ} (from POV of L)
 turn off all INDEP. sources



Assignment Project Exam Help

$$R_{EQ} = 20 \Omega \quad \tau = \frac{L}{R_{EQ}} = \frac{0.2}{20} = 0.01$$

<https://powcoder.com>

$$i_L(t) = i_L(\infty) + [i_L(0) - i_L(\infty)] e^{-t/\tau}$$

$$i_L(t) = 0.4 + [0 - 0.4] e^{-t/0.01}$$

Add WeChat powcoder


$$i_L(t) = 0.4 (1 - e^{-100t}) \text{ A}$$

$$v_L(t) = L \frac{di_L(t)}{dt} = 0.2 \times [0.4 (0 - e^{-100t} \times (-100))] = 8e^{-100t} \text{ V}$$

$$v_L(t) = 0.2 \times 0.4 \times 100 e^{-100t} = 8e^{-100t} \text{ V}$$


$$v_L(0) = 8 \text{ V}$$

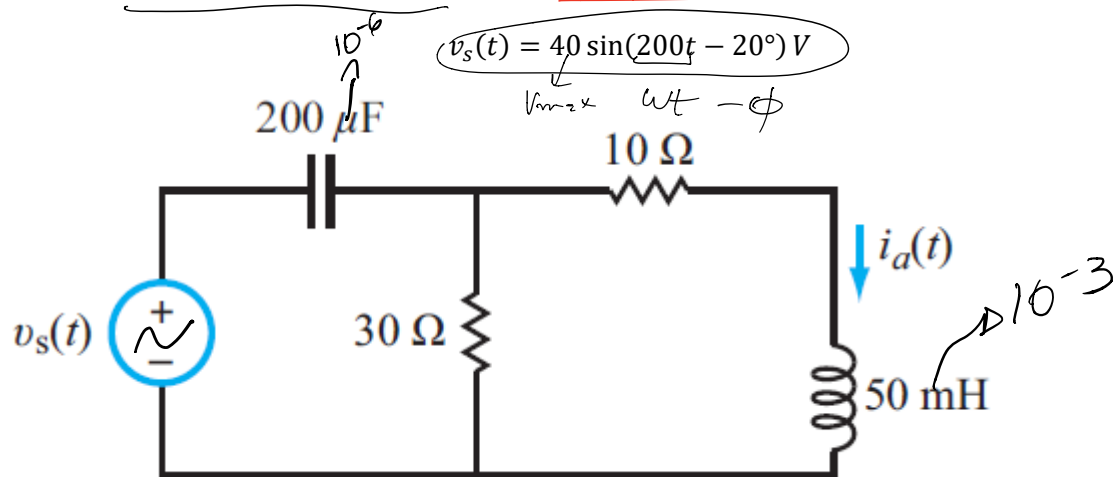Find the current through the inductor and the power delivered by the source.



$$v_s(t) = 40 \cos(200t - 110^\circ) V$$

Assignment Project Exam Help

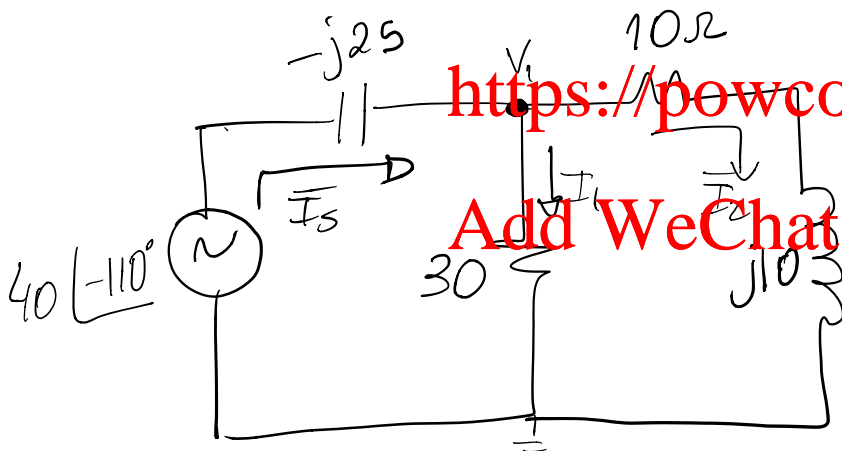

<https://powcoder.com>

Add WeChat powcoder

$$Z_R = R$$

$$Z_L = j\omega L$$

$$Z_L = j \times 200 \times 50 \times 10^{-3}$$


$$Z_L = j10$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j200 \times 200 \times 10^{-6}} = -j25$$


$$Z_{eq} = (10 + j10) \parallel 30 + (-j25)$$

$$Z_{eq} = \frac{(10 + j10) \times 30}{40 + j10} + (-j25)$$

$$Z_{eq} = 21.6 \angle -65.87^\circ$$

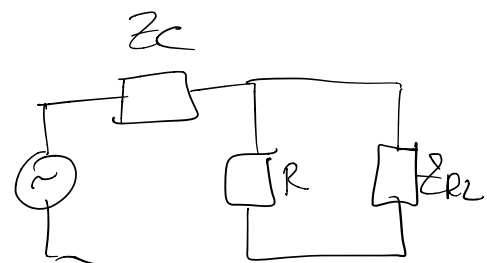
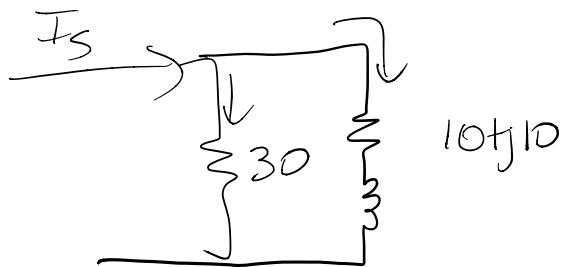
$$\bar{I}_S = \frac{V_S}{Z_{eq}} = \frac{40 \angle -110^\circ}{21.6 \angle -65.87^\circ} = 1.85 \angle -44.12^\circ \text{ A}$$



current division:

$$\bar{I}_2 = \frac{\bar{I}_S \times 30}{40 + j10} = 1.34 \angle -58.15^\circ \text{ A}$$

Assignment Project Exam Help

$$i_L(t) = 1.34 \cos(200t - 58.15^\circ) \text{ A}$$

<https://powcoder.com>

$$\bar{S}_S = \frac{\bar{V}_S \bar{I}_S^*}{2} = \frac{40 \angle -110^\circ \times 1.85 \angle +44.12^\circ}{2}$$

Add WeChat powcoder

$$\bar{S}_S = 37 \angle -65.88^\circ = 15.12 - j33.77 \text{ VA}$$



$$P = 15.12 \text{ W} \quad Q = 33.77 \text{ VAR}$$

$$\text{pf} = \frac{P}{S} = \frac{15.12}{37} = 0.4$$


$$\text{pf} = \cos(\theta_V - \theta_I) = \cos(-65.88) = 0.4$$

power angle
imped angle

pf = 0.4 leading

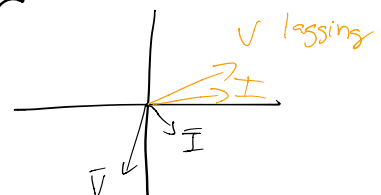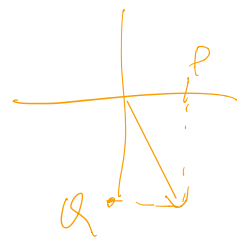

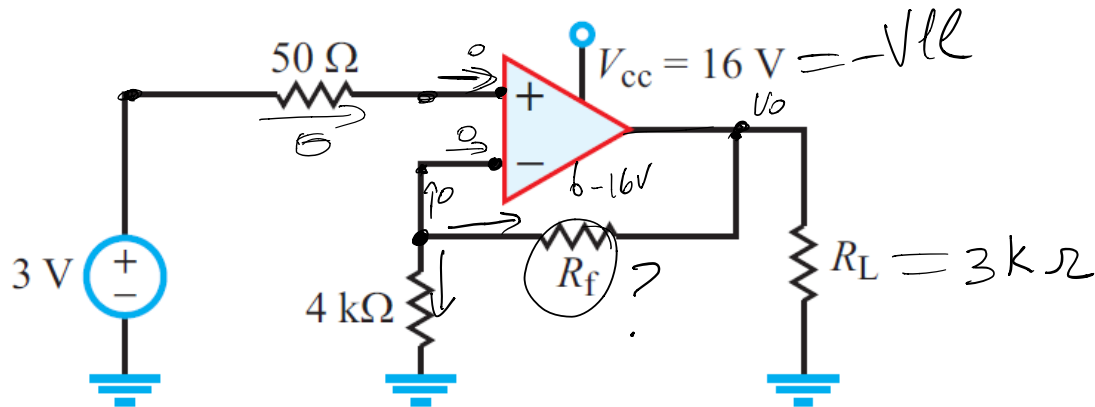The supply voltage of the op amp is 16 V. If $R_L = 3\text{ k}\Omega$, find R_f such that the circuit delivers 75 mW of power to R_L .



$$\frac{V_o^2}{R_L} = P_{out} = 75 \times 10^{-3} \text{ W} \Rightarrow V_o = \sqrt{3 \times 10^3 \times 75 \times 10^{-3}} = 15 \text{ V} < 16 \text{ V} \checkmark$$

Assignment Project Exam Help
<https://powcoder.com>

$V^+ = V^- = 3 \text{ V}$ **Add WeChat powcoder**

KVL @ V^- : $\frac{V^- - 0}{4\text{ k}} + \frac{V^- - V_o}{R_f} + 0 = 0$


$$\frac{3}{4\text{ k}} + \frac{3 - 15}{R_f} = 0 \Rightarrow \frac{12}{R_f} = \frac{3}{4 \times 10^3} \Rightarrow R_f = 16 \text{ k}\Omega$$

OR: recognize it's a non-inverting amplifier:

$$V_o = \left(\frac{R_1 + R_2}{R_2} \right) v_s \Rightarrow \underset{15}{V_o} = \left(\frac{4\text{ k} + R_f}{R_f} \right) \underset{3}{v_s}$$

find $R_f = 16 \text{ k}\Omega$

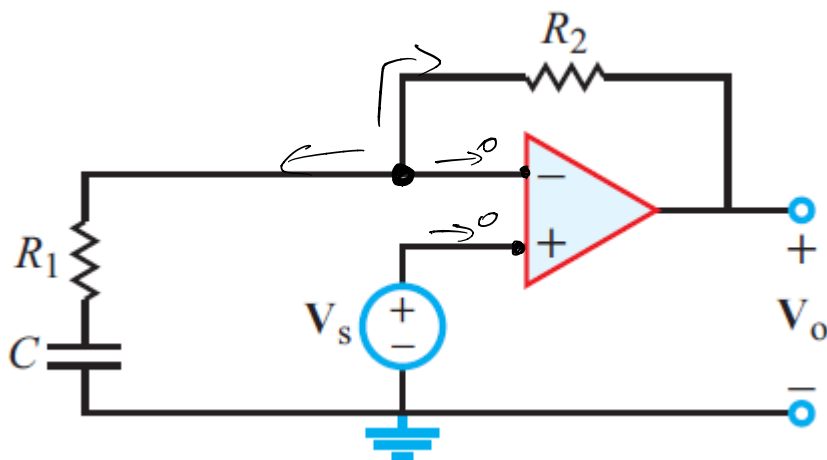Obtain an expression for $H(\omega) = V_o/V_s$.



$$V^- = V^+ = V_s$$

KCL @ V^- : $\frac{V_s - 0}{R_1 + \frac{1}{j\omega C}} + \frac{V_s - V_o}{R_2} + 0 = 0$

<https://powcoder.com>

Add WeChat powcoder



$$V_s \left(\frac{1}{R_1 + \frac{1}{j\omega C}} + \frac{1}{R_2} \right) = \frac{V_o}{R_2}$$

$$\frac{V_o}{V_s} = R_2 \left[\frac{1}{R_1 + \frac{1}{j\omega C}} + \frac{1}{R_2} \right] = \cancel{R_2} \left[\frac{R_2 + R_1 + \frac{1}{j\omega C}}{\cancel{R_2} \left(R_1 + \frac{1}{j\omega C} \right)} \right] \times j\omega C$$

$$= \frac{R_2 j\omega C + R_1 j\omega C + 1}{R_1 j\omega C + 1} = \frac{1 + (R_1 + R_2)j\omega C}{1 + jR_1\omega C}$$

filter

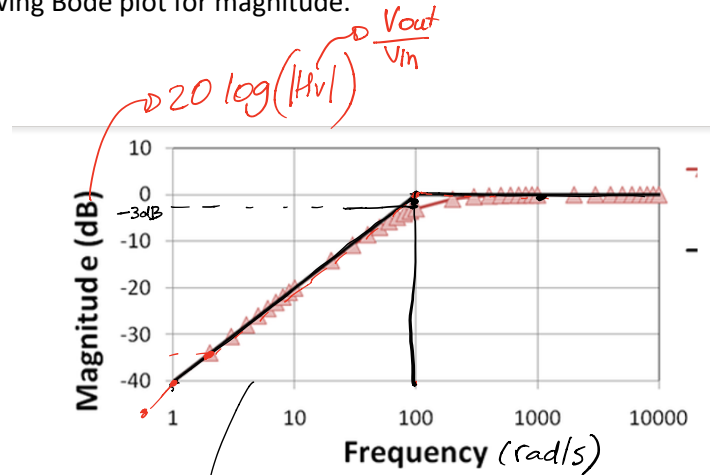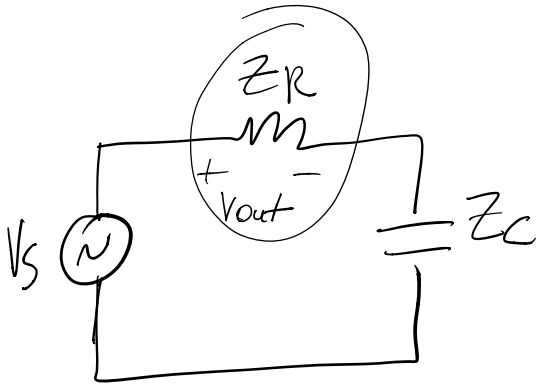Design the circuit below to be a ~~HPF~~ with the following Bode plot for magnitude.



HPF

$$\frac{V_R}{V_S} = \frac{Z_R}{Z_R + Z_C} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 - j\frac{\omega C}{R}}$$

$$\omega \rightarrow 0 : \frac{V_R}{V_S} \rightarrow 0$$

$$\omega \rightarrow \infty : \frac{V_R}{V_S} \rightarrow 1$$

Assignment Project Exam Help

We need to choose

<https://powcoder.com>

output as the voltage through the resistor.

Add WeChat powcoder

$$\frac{V_C}{V_S} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega RC + 1}$$

$$\omega \rightarrow 0 : \frac{V_R}{V_S} = 1$$

$$\omega \rightarrow \infty : \frac{V_R}{V_S} = 0$$

LPF

$$H_V(\omega) = \frac{1}{1 - j\frac{\omega C}{R}} = \frac{1}{1 - j\frac{\omega C}{R}}$$

$$\omega C \rightarrow \frac{P_{out}}{P_{in}} = \frac{1}{2} \Rightarrow |H_V| = \frac{1}{\sqrt{2}}$$

$$\omega_c = 100 \text{ rad/s}$$

$$\omega_c = \frac{1}{RC} = 100$$

$$\text{so, } \frac{1}{C} = 100R$$

$$C = 1 \times 10^{-6} \text{ F} = 1 \mu\text{F}$$

$$R = 10 \text{ k}\Omega$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder